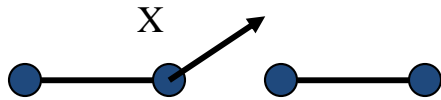



Preliminaries

- Before we get into the design of computers and their components, we must understand the basics of Boolean algebra.
- The knowledge of Boolean algebra will enable you to specify and optimize your computer design(s)

Switching Theory




$X = 0 \rightarrow$ Switch open

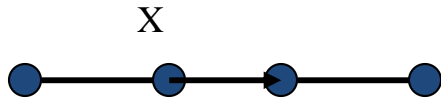

$X = 1 \rightarrow$ Switch closed


Switching Theory

(The AND Gate)

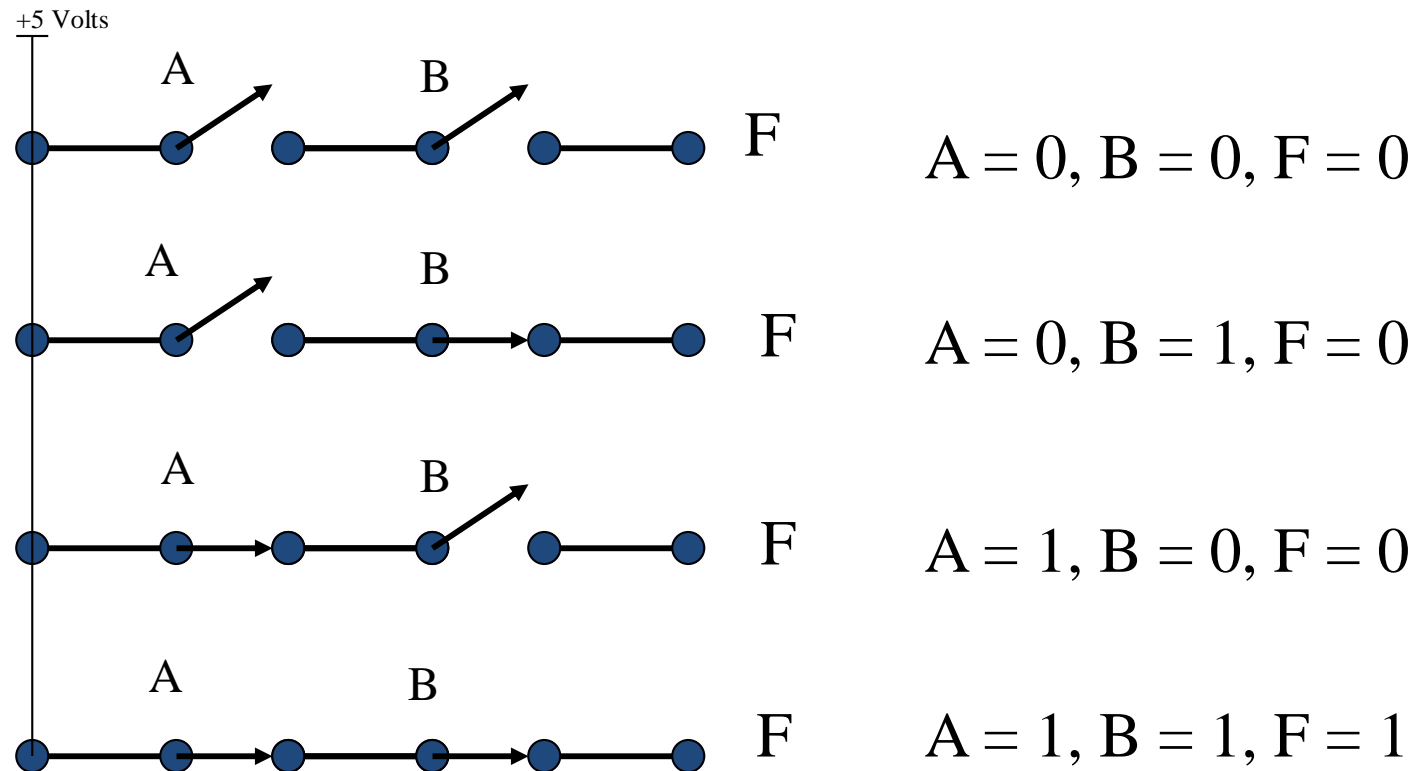

Switching Theory

(The OR Gate)

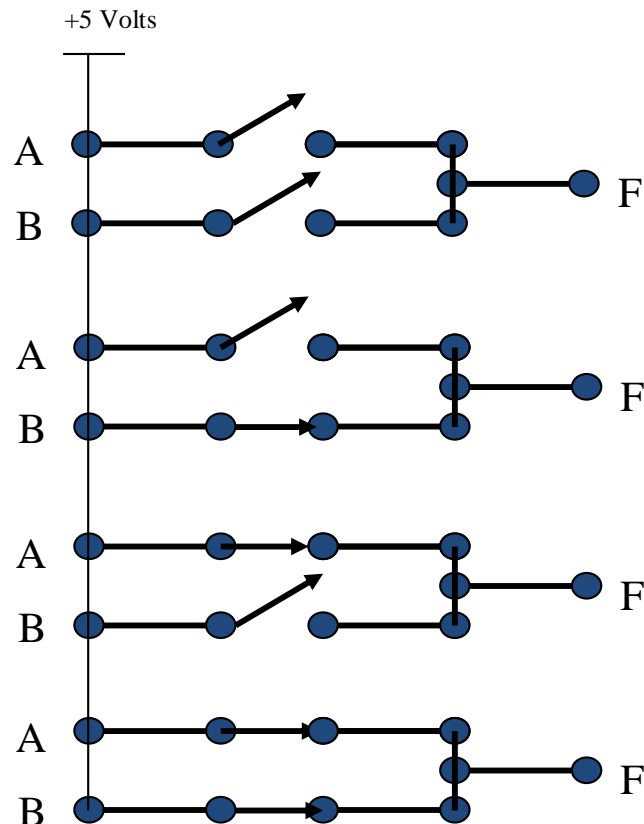

$$A = 0, B = 0, F = 0$$

$$A = 0, B = 1, F = 1$$

$$A = 1, B = 0, F = 1$$

$$A = 1, B = 1, F = 1$$

Symbolic Representations of Logic Functions

- There are more intuitive ways to represent logic functions than by the use of switches
- Each of the basic logic functions have symbolic representations that are universally understood
- These basic representations are referred to as logic gates

Boolean Functions

- $+$ \rightarrow The OR function
- $'$ \rightarrow The NOT function
- \bullet \rightarrow The AND function
- \oplus \rightarrow The XOR function

Logic Gates

- Each Boolean function has a corresponding symbolic representation.
- These symbolic representations are commonly referred to as logic gates

Truth Tables

- Truth tables specify values of a Boolean expression for all possible combinations of variables in the expression
- Each of the basic logic gates, for instance has a set of inputs. The respective truth tables for each gate shows the behavior of the gate's output for all possible input combinations.


Truth Tables for Logic Gates

AND




A	B	$A \bullet B$
0	0	0
0	1	0
1	0	0
1	1	1

OR

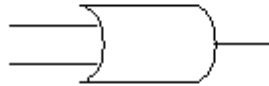

A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

XOR

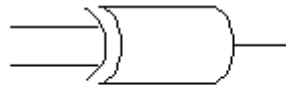

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

Truth Tables for Logic Gates

NOT



A	\bar{A}
0	1
1	0


Truth Tables for Logic Gates

NAND



A	B	$\overline{(A \bullet B)}$
0	0	1
0	1	1
1	0	1
1	1	0

NOR

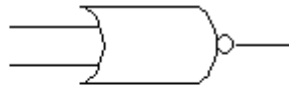

A	B	$\overline{(A + B)}$
0	0	1
0	1	0
1	0	0
1	1	0

XNOR



A	B	$\overline{(A \oplus B)}$
0	0	1
0	1	0
1	0	0
1	1	1

Exercise I

Draw the logic gates and generate the truth tables for the following expressions:


1. $F = A + BC$

2. $F = AB' + A'B$

3. $F = A+B+AC$


Exercise 1: Solution 1

$$F = A + BC$$

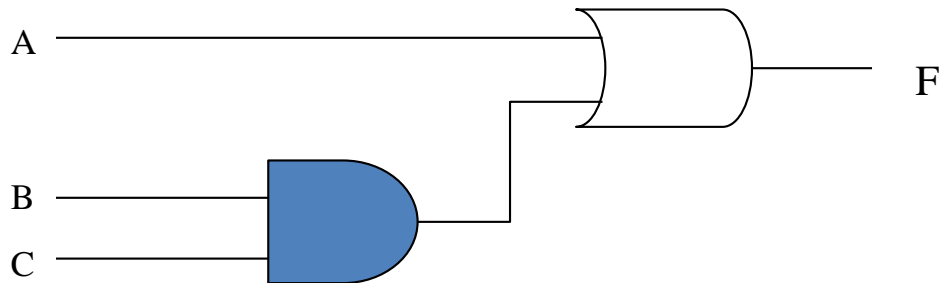


Exercise 1: Solution 2

$$F = AB' + A'B$$

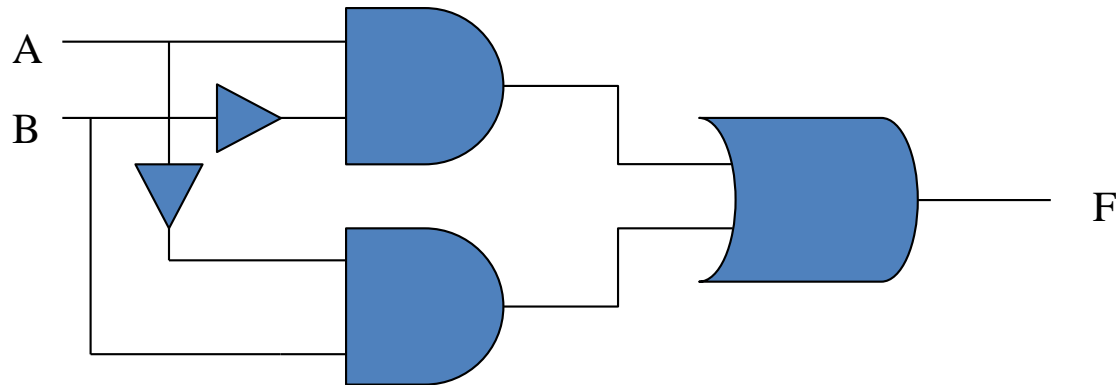

Exercise 1: Solution 3

$$F = A + B + AC$$

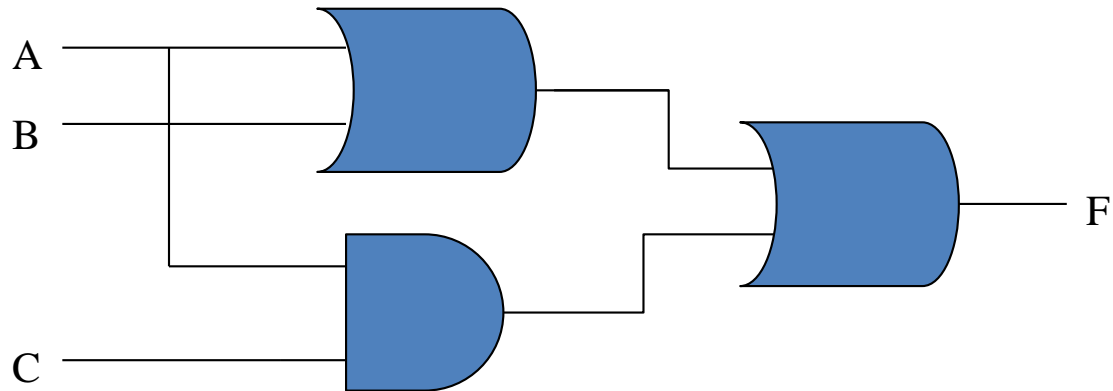

Basic Theorems of Boolean Algebra

$$X + 0 = X$$

$$X \cdot 1 = X$$

$$X + 1 = 1$$

$$X \cdot 0 = 0$$

Idempotent Laws

$$X + X = X$$

$$X \cdot X = X$$

Involution Law

$$(X')' = X$$

Laws of Complementarity

$$X + X' = 1$$

$$X \cdot X' = 0$$

Commutative, Associative and Distributive Laws

A lot of the laws of ordinary algebra are valid for Boolean algebra:

Commutative Law: $A+B = B+A$ $AB = BA$

Associative Law: $(A+B)+C = A+(B+C)$ $(AB)C = A(BC)$

Distributive Law: $A(B+C) = AB + AC$

Second Distributive Law: $A + BC = (A+B)(A+C)$

Note: This law does not hold for ordinary algebra.

Simplification Theorems

These theorems are very helpful in simplifying Boolean expressions:

1. $AB + AB' = A$
2. $(A+B)(A+B') = A$
3. $A + AB = A$
4. $A(A+B) = A$
5. $(A+B')B = AB$
6. $AB' + B = A + B$

Simplification Theorems

Proof of Theorem 1

1. $AB + AB' = A$

$$A(B + B') = A(1) = A$$

Simplification Theorems

Proof of Theorem 2

$$\begin{aligned} 2. (A+B)(A+B') &= A \\ AA + AB' + AB + BB' & \\ A + A(B'+B) + 0 & \\ A + A &= A \end{aligned}$$

Simplification Theorems

Proof of Theorem 3

$$\begin{aligned} 3. \quad & A + AB = A \\ & A(1 + B) \\ & A(1) = A \end{aligned}$$

Simplification Theorems

Proof of Theorem 4

$$4. A(A+B) = A$$

$$AA + AB$$

$$A + AB$$

$$A(1+B)$$

$$A(1) = A$$

Simplification Theorems

Proof of Theorem 5

$$\begin{aligned} 5. (A+B')B &= AB \\ AB + BB' & \\ AB + 0 &= AB \end{aligned}$$

Simplification Theorems

Proof of Theorem 6

$$\begin{aligned} 6. \quad & AB' + B = A + B \\ & B + AB' = A + B \\ & (B + A)(B + B') \\ & (B + A)(1) = B + A = A + B \end{aligned}$$