

# Tutorial: Overview of Boolean Algebra and Logic


Yul Williams, D.Sc.

# Outline

- Digital Logic
- Boolean Algebra
- Boolean Functions
- DeMorgan's Law
- Minterms and Maxterms
- Logic Minimization – The Karnaugh Map


# Digital Logic

# Data Representation

 

Analog signals are continuous and can take on a wide variety of values at specific intervals in time.

# Data Representation

 

# Digital Systems

- In a digital system the physical signals may only assume discrete values.
- As shown in the previous figure, the digital signal may either be 0 volts or +5 volts
- Most components in a digital system assume only two discrete values

# Digital Logic Levels

If:  $V = 0$  volts, then it is referred to as Logic '0' or Logic "Lo"


If:  $V = 5$  volts, then it is referred to as Logic '1' or Logic "Hi"

# Boolean Algebra

It's George's Fault!!



# George Boole

 


(1815-1864)

Mathematician and logician who developed ways of expressing logical processes using algebraic symbols, creating a branch of mathematics known as symbolic logic. Today, we call this Boolean Logic.


# Preliminaries

- Before we get into the design of computers and their components, we must understand the basics of Boolean algebra.
- The knowledge of Boolean algebra will enable you to specify and optimize your computer design(s)

# Switching Theory

 


$X = 0 \rightarrow$  Switch open

 

$X = 1 \rightarrow$  Switch closed


# Switching Theory

## (The AND Gate)

 

# Switching Theory

## (The OR Gate)

 

$$A = 0, B = 0, F = 0$$

$$A = 0, B = 1, F = 1$$

$$A = 1, B = 0, F = 1$$

$$A = 1, B = 1, F = 1$$

# Boolean Functions

Mathematical and Symbolic  
Representations

# Symbolic Representations of Logic Functions

- There are more intuitive ways to represent logic functions than by the use of switches
- Each of the basic logic functions have symbolic representations that are universally understood
- These basic representations are referred to as logic gates

# Boolean Functions



- $+$   $\rightarrow$  The OR function
- $'$   $\rightarrow$  The NOT function
- $\cdot$   $\rightarrow$  The AND function
- $\oplus$   $\rightarrow$  The XOR function



# Logic Gates

- Each Boolean function has a corresponding symbolic representation.
- These symbolic representations are commonly referred to as logic gates

# Logic Gates

  


# Truth Tables

- Truth tables specify values of a Boolean expression for all possible combinations of variables in the expression
- Each of the basic logic gates, for instance has a set of inputs. The respective truth tables for each gate shows the behavior of the gate's output for all possible input combinations.


# Truth Tables for Logic Gates

AND

 


A	B	$A \bullet B$
0	0	0
0	1	0
1	0	0
1	1	1

OR

 

A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

XOR

 

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

# Truth Tables for Logic Gates


NOT



A	$\bar{A}$
0	1
1	0


# Truth Tables for Logic Gates

NAND

 

A	B	$\overline{(A \bullet B)}$
0	0	1
0	1	1
1	0	1
1	1	0

NOR

 

A	B	$\overline{(A + B)}$
0	0	1
0	1	0
1	0	0
1	1	0

XNOR



A	B	$\overline{(A \oplus B)}$
0	0	1
0	1	0
1	0	0
1	1	1

# Exercise I

Draw the logic gates and generate the truth tables for the following expressions:

1.  $F = A + BC$

2.  $F = AB' + A'B$

3.  $F = A+B+AC$

# Basic Theorems of Boolean Algebra

$$X + 0 = X$$

$$X \cdot 1 = X$$

$$X + 1 = 1$$

$$X \cdot 0 = 0$$

Idempotent Laws

$$X + X = X$$

$$X \cdot X = X$$

Involution Law

$$(X')' = X$$

Laws of Complementarity

$$X + X' = 1$$

$$X \cdot X' = 0$$



# Commutative, Associative and Distributive Laws

A lot of the laws of ordinary algebra are valid for Boolean algebra:

Commutative Law:  $A+B = B+A$                        $AB = BA$

Associative Law:  $(A+B)+C = A+(B+C)$      $(AB)C = A(BC)$

Distributive Law:  $A(B+C) = AB + AC$

Second Distributive Law:  $A + BC = (A+B)(A+C)$

Note: This law does not hold for ordinary algebra.

# Simplification Theorems

These theorems are very helpful in simplifying Boolean expressions:

1.  $AB + AB' = A$
2.  $(A+B)(A+B') = A$
3.  $A + AB = A$
4.  $A(A+B) = A$
5.  $(A+B')B = AB$
6.  $AB' + B = A + B$

# Simplification Theorems

## Proof of Theorem 1

1.  $AB + AB' = A$

$$A(B + B') = A(1) = A$$

# Simplification Theorems

## Proof of Theorem 2

$$\begin{aligned} 2. (A+B)(A+B') &= A \\ AA + AB' + AB + BB' & \\ A + A(B'+B) + 0 & \\ A + A &= A \end{aligned}$$

# Simplification Theorems

## Proof of Theorem 3

$$\begin{aligned} 3. \quad & A + AB = A \\ & A(1 + B) \\ & A(1) = A \end{aligned}$$

# Simplification Theorems

## Proof of Theorem 4

$$4. A(A+B) = A$$

$$AA + AB$$

$$A + AB$$

$$A(1+B)$$

$$A(1) = A$$

# Simplification Theorems

## Proof of Theorem 5

$$\begin{aligned} 5. (A+B')B &= AB \\ AB + BB' & \\ AB + 0 &= AB \end{aligned}$$

# Simplification Theorems

## Proof of Theorem 6

$$\begin{aligned} 6. \quad & AB' + B = A + B \\ & B + AB' = A + B \\ & (B + A)(B + B') \\ & (B + A)(1) = B + A = A + B \end{aligned}$$



# DeMorgan's Law

# Augustus De Morgan



( 1806 - 1871 )

He recognized the purely symbolic nature of algebra and he was aware of the existence of algebras other than ordinary algebra. He introduced **De Morgan's laws** and his greatest contribution is as a reformer of mathematical logic.

# Logic Equivalence

- DeMorgan's Law allows us to convert an AND function into an equivalent OR function (and vice versa)

DeMorgan's Law may be expressed by the following equivalent equations:

$$(ab)' = a' + b'$$

$$(a + b)' = a'b'$$

# DeMorgan's Law

- DeMorgan's Law (in general):

$$(a+b+c+\dots)' = a'b'c'\dots$$

$$(abc\dots)' = a'+b'+c'+\dots$$

# Minterms and Maxterms

# Minterms

- A minterm of  $n$  variables is a product of  $n$  literals in which each variable appears exactly once in either true or complimented form (but not both)

ABC	Minterms	Designator
000	$A'B'C'$	$= m_0$
001	$A'B'C$	$= m_1$
010	$A'BC'$	$= m_2$
011	$A'BC$	$= m_3$
100	$AB'C'$	$= m_4$
101	$AB'C$	$= m_5$
110	$ABC'$	$= m_6$
111	$ABC$	$= m_7$

A Boolean expression such as:  $F = ABC + A'B'C + AB'C$  is expressed as a sum of products. In addition, it may be expressed using the designator representation (or m-notation).

$$F(A,B,C) = m_1 + m_5 + m_7$$

OR

$$F(A,B,C) = \sum m(1, 5, 7)$$

When examining a truth table for a given expression, the minterms correspond to the 1's in F.

# Maxterms

- A maxterm of  $n$  variables is a sum of  $n$  literals in which each variable appears exactly once in either true or complimented form (but not both)

ABC	Maxterms	Designator
000	$A+B+C$	$= M_0$
001	$A+B+C'$	$= M_1$
010	$A+B'+C$	$= M_2$
011	$A+B'+C'$	$= M_3$
100	$A'+B+C$	$= M_4$
101	$A'+B+C'$	$= M_5$
110	$A'+B'+C$	$= M_6$
111	$A'+B'+C'$	$= M_7$

A Boolean expression such as:  $F = (A+B+C)(A'+B'+C)(A+B'+C)$  is expressed as a product of sums. In addition, it may be expressed using the designator representation (or M-notation).

$$F(A,B,C) = M_0 M_2 M_6$$

OR

$$F(A,B,C) = \prod M(0, 2, 6)$$

When examining a truth table for a given expression, the maxterms correspond to the 0's in F.

# Logic Minimization

## The Karnaugh Map



# Cost as a Function of Logic

- Each logic design will consist of a number of logic gates. Each gate that is a part of the resulting design adds cost to the design.
- The goal of logic minimization is to perform the logic function while minimizing the number of required gates (thus reducing the cost).
  - One way to solve this problem is to use the algebraic techniques that we just learned
  - Another way is to use a tool called the **Karnaugh Map**

# The Karnaugh Map

- Used to minimize logic functions
  - Logic functions may be minimized using an algebraic
- Many logic functions may be plotted on a Karnaugh map (sometimes called a K-map)
- Mapping functions containing more than 6 variables becomes difficult with Karnaugh maps

# 2-Variable K-Maps

Initial Function:


$$F = AB + A'B$$

Truth Table for F:

AB	F
00	0
01	1
11	1
10	0

K-Map

	A	0	1
B	0	0	0
1	1	1	

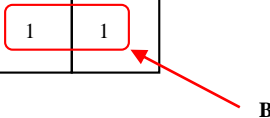

Algebraic Simplification of

F

$$\begin{aligned} F &= AB + A'B \\ &= B(A + A') \\ &= B(1) \\ &= B \end{aligned}$$

$$F = B$$

Minimized Function

# The Gray Code

0	0	0	00	000
1	1	1	01	001
		-----	11	011
		1	10	010
		0		-----
				110
				111
				101
				100

Notice that only a single digit is different from the number preceding or succeeding a specific number in the code sequence. These numbers are said to be adjacent to each other.

**Karnaugh maps are constructed using Gray codes . This is an important concept because this property helps to identify redundant terms in logic expressions so they may be systematically eliminated.**

# 3-Variable K-Maps

Initial Function:

$$F = ABC + A'BC + A'B'C$$

Truth Table for F:

ABC	F
000	0
001	1
010	0
011	1
100	0
101	0
110	0
111	1

K-Map

	A	0	1
BC			
00		0	0
01		1	0
11		1	1
10		0	0

Red arrows indicate groupings:  $A'C$  (vertical group of 1s in column A=0) and  $BC$  (horizontal group of 1s in row B=1).

$$F = A'C + BC$$

Minimized Function

Algebraic Simplification of

F

$$F = ABC + A'BC + A'B'C$$

$$= C(AB + A'B + A'B')$$

$$= C(AB + A' + B)$$

$$= C(B(A + 1) + A')$$

$$= C(B + A')$$

$$= BC + A'C$$

$$= A'C + BC$$


# 4-Variable K-Maps

Truth Table for F:

ABCD	F
0000	1
0001	0
0010	1
0011	0
0100	1
0101	1
0110	1
0111	1
1000	1
1001	0
1010	1
1011	1
1100	1
1101	0
1110	1
1111	1

Initial Function F:
 
$$F = A'B'C'D' + A'B'CD' + A'BC'D' + A'BC'D + A'BCD' + A'BCD + AB'C'D' + AB'CD' + AB'CD + ABC'D' + ABCD' + ABCD$$



The term  $ACD$  is a non-optimal grouping cause an extra term to be produced that adds no value to the valuation of the equation. Take the green grouping instead that yields the term  $AC$ .

$$F = AC + A'B + D'$$

Minimized Function

# Practice Questions

1. Prove the following:

$$cd + cd' = c$$

$$(x+y)(x+y') = x$$

$$(a+x)(a+y) = a + xy$$

2. Draw the logic network for the following Boolean expressions:

$$a + bc + d$$

$$ab(c + d)$$

$$(ab + b'c + a'c')d$$

3. Draw the Karnaugh map and find the minimum sum of products for the function:  $F = b'c' + a'bd + abcd' + b'c$

4. Draw the Karnaugh map and find the minimum product of sums for the function F in problem 3.